

VIETNAM NATIONAL UNIVERSITY HO CHI MINH CITY  
HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY  
FACULTY OF COMPUTER SCIENCE AND ENGINEERING



## Electrical Electronic Circuits

---

### Lab Report

## Lab 6

---

Advisor(s): Phạm Công Thái

Student(s): Nguyễn Phúc Vĩnh 2414001

Trần Văn Minh Triết 2413603

HO CHI MINH CITY, DECEMBER 2025



**Contents**

**1 Introduction** **1**

**2 Junction Field Effect Transistor** **2**

**3 Metal Oxide Semiconductor FET** **3**

    3.1 Depletion-mode MOSFET . . . . . 3

    3.2 Enhancement-mode MOSFET . . . . . 5

**List of Figures**

    3.1 DFET verification in PSPICE . . . . . 3

    3.2 Simulation results with DFET . . . . . 4

    3.3 Self bias configuration for DFET . . . . . 4

    3.4 Simulation results . . . . . 5

    3.5 EFET validation . . . . . 6

    3.6 Simulation results with EFET . . . . . 6

**List of Tables**

**Listings**



# 1 Introduction

In the Bipolar Junction Transistor tutorials, we saw that the output Collector current of the transistor is proportional to input current flowing into the Base terminal of the device, thereby making the bipolar transistor a **CURRENT** operated device (Beta model) as a smaller current can be used to switch a larger load current.

The Field Effect Transistor, or simply FET however, uses the voltage that is applied to their input terminal, called the Gate to control the current flowing through them resulting in the output current being proportional to the input voltage. As their operation relies on an electric field (hence the name field effect) generated by the input Gate voltage, this then makes the Field Effect Transistor a **VOLTAGE** operated device.

The Field Effect Transistor has one major advantage over its standard bipolar transistor cousins, in that their input impedance, ( $R_{in}$ ) is very high, (thousands of Ohms), while the BJT is comparatively low. This very high input impedance makes them very sensitive to input voltage signals, but the price of this high sensitivity also means that they can be easily damaged by static electricity.



## 2 Junction Field Effect Transistor

### 3 Metal Oxide Semiconductor FET

As well as the Junction Field Effect Transistor (JFET), there is another type of Field Effect Transistor available whose Gate input is electrically insulated from the main current carrying channel and is therefore called an Insulated Gate Field Effect Transistor.

The most common type of insulated gate FET which is used in many different types of electronic circuits is called the Metal Oxide Semiconductor Field Effect Transistor or MOS-FET for short.

The IGFET or MOSFET is a voltage controlled field effect transistor that differs from a JFET in that it has a "Metal Oxide" Gate electrode which is electrically insulated from the main semiconductor n-channel or p-channel by a very thin layer of insulating material usually silicon dioxide, commonly known as glass.

#### 3.1 Depletion-mode MOSFET

The Depletion-mode MOSFET, which is less common than the enhancement mode types. This device is very similar to JFET, except that the maximum current saturation is obtained at  $V_{GS} > 0$ . The circuit used to verify  $I_{DSS}$  and  $V_P$  for DFET is presented as follows:

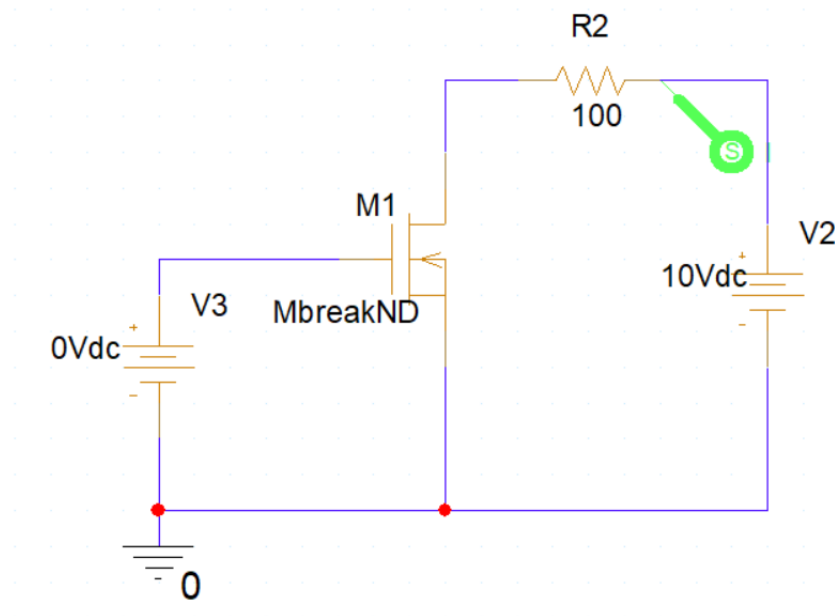


Figure 3.1: DFET verification in PSPICE

The device for a common DFET is MbreakND. After a dc sweep simulation when V3

varies from -5V to 0V, the results are shown below:

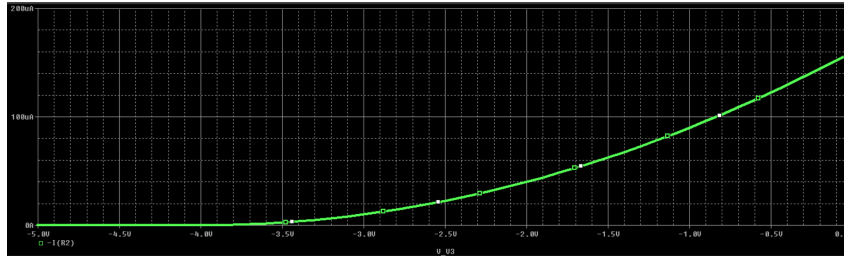


Figure 3.2: Simulation results with DFET

From this simulation results, it is confirmed that  $IDSS = 160\text{mA}$  and  $V_P = -4$  for DFET.

Students are proposed to implement the circuit below:

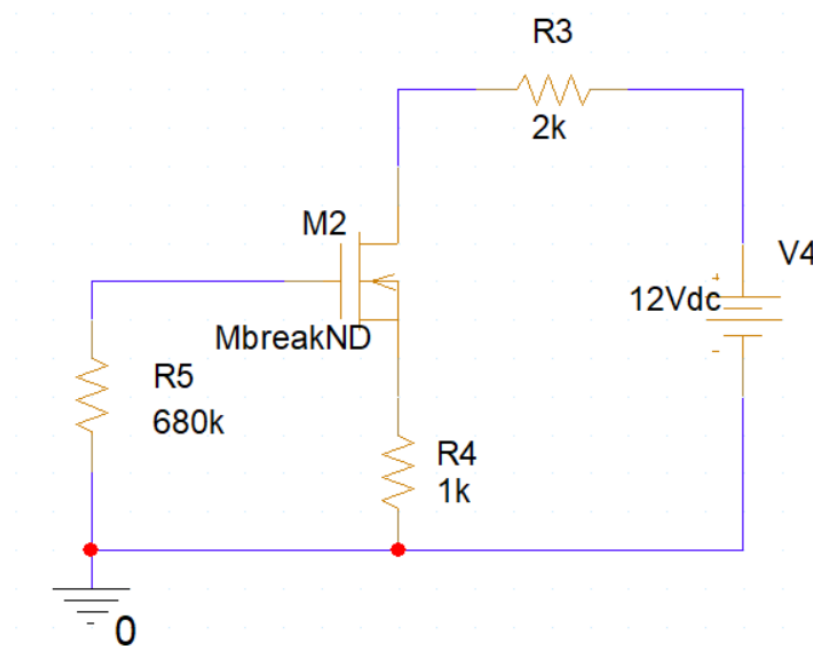


Figure 3.3: Self bias configuration for DFET

Only the bias configuration is required to executed. Please capture the simulation results with current and voltage information on the circuit. Finally, explain these values by theory calculations.

**Simulation results:**

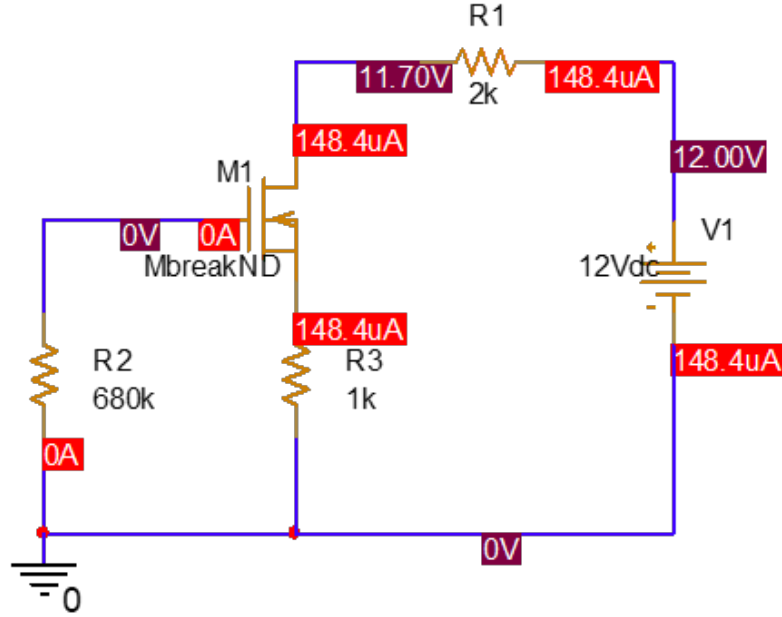


Figure 3.4: Simulation results

#### Explanation:

In this circuit, the Depletion-mode MOSFET (MbrcakND) is biased using the self-bias configuration. The gate terminal is connected to ground through a very large resistor  $R_2 = 680\text{ k}\Omega$ , therefore the gate voltage is fixed at:

$$V_G = 0\text{ V}$$

The drain current  $I_D$  flows through the source resistor  $R_3 = 1\text{ k}\Omega$ , creating a voltage drop at the source:

$$V_S = I_D \cdot R_3 = 148.4\text{ }\mu\text{A} \times 1\text{ k}\Omega = 0.148\text{ V}$$

As a result, the gate-to-source voltage becomes:

$$V_{GS} = V_G - V_S = 0 - 0.148 = -0.148\text{ V}$$

This negative  $V_{GS}$  is generated automatically by the circuit due to the voltage drop across the source resistor and is the key mechanism of the self-bias operation. The negative  $V_{GS}$  reduces the drain current and stabilizes the operating point of the DFET without requiring an external negative power supply.

The drain voltage can be calculated as:



$$V_D = V_{DD} - I_D \cdot R_1 = 12 - 148.4 \mu A \times 2 k\Omega \approx 11.70 V$$

The simulation results give  $I_D = 148.4 \mu A$  and  $V_D = 11.70 V$ , which are in full agreement with the theoretical analysis. Therefore, the DFET operates correctly in the saturation (active) region with a stable self-bias operating point.

### 3.2 Enhancement-mode MOSFET

The more common Enhancement-mode MOSFET or eMOSFET. The device is normally “OFF” (non-conducting) when the gate bias voltage,  $V_{GS}$  is equal to zero. For the n channel enhancement MOS transistor a drain current will only flow when a gate voltage (  $V_{GS}$  ) is applied to the gate terminal greater than the threshold voltage (  $V_{TH}$  ) level in which conductance takes place making it a transconductance device. In other words, for an n-channel enhancement mode MOSFET:  $+V_{GS}$  turns the transistor “ON”, while a zero or  $-V_{GS}$  turns the transistor “OFF”. Thus the enhancement-mode MOSFET is equivalent to a “normally-open” switch.

The reverse is true for the p-channel enhancement MOS transistor. When  $V_{GS} = 0$  the device is “OFF” and the channel is open. The application of a negative (-ve) gate voltage to the p-type eMOSFET enhances the channels conductivity turning it “ON”. Then for an p- channel enhancement mode MOSFET:  $+V_{GS}$  turns the transistor “OFF”, while  $-V_{GS}$  turns the transistor “ON”.

The validation of an EFET in PSPICE is presented bellow. The typical EFET in PSPICE is **MbreakN** device.

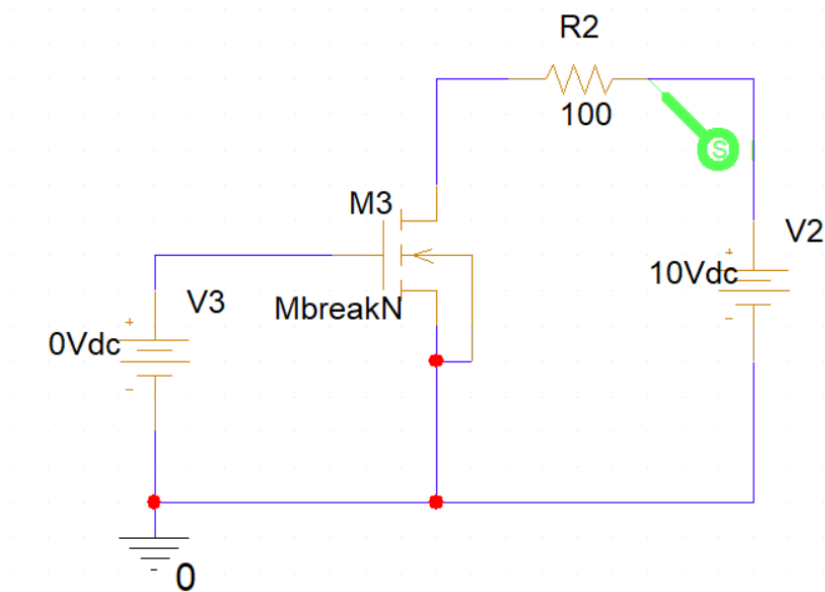


Figure 3.5: EFET validation

A dc sweep simulation with V3 can be performed. The simulation results with V3 varies from -1V to 5V are presented as following:

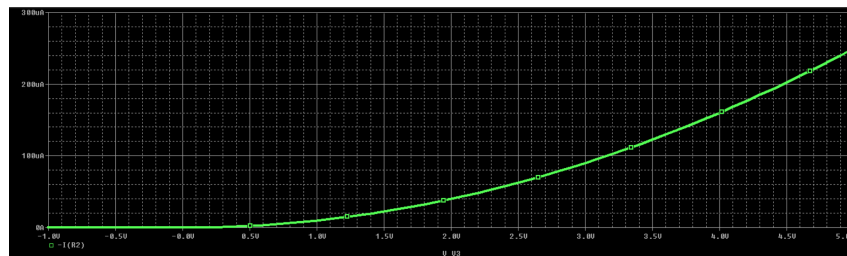


Figure 3.6: Simulation results with EFET